



Figure 6: Experimental resistances, currents, and voltages for complex circuit.