

Circuit Lab

Kade Jorud, Connor LaSota, and Luke Tollefson

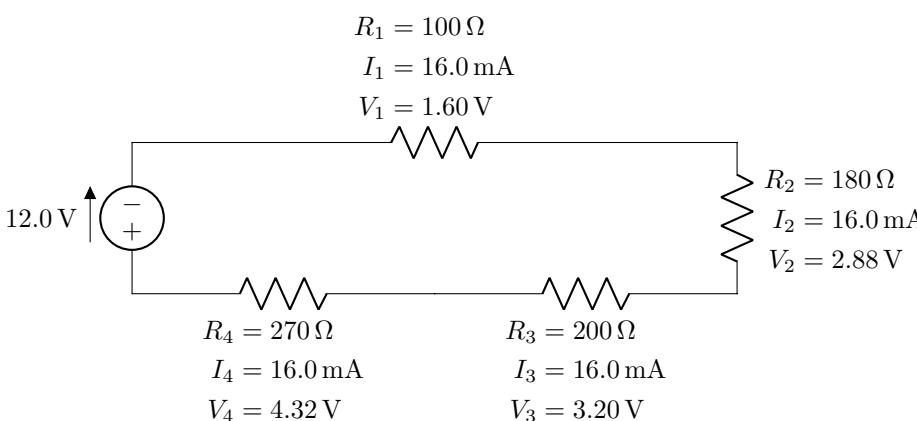


Figure 1: Predicted currents and voltages for series circuit.

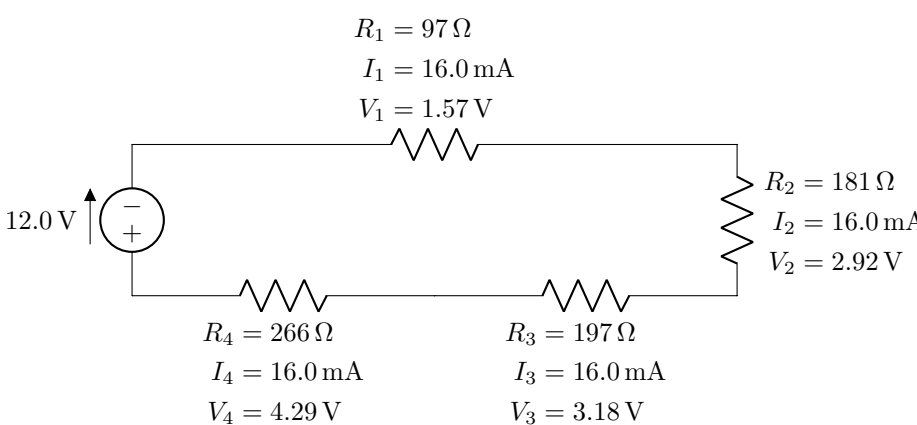


Figure 2: Experimental resistances, currents, and voltages for series circuit.

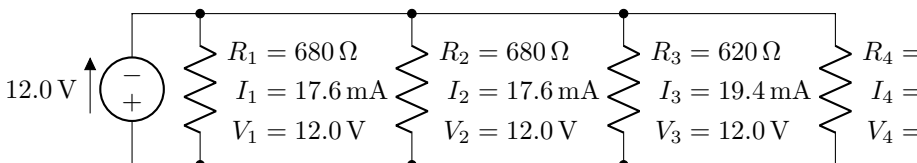


Figure 3: Predicted currents and voltages for parallel circuit.

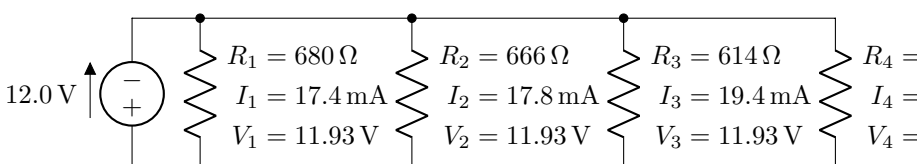


Figure 4: Experimental resistances, currents, and voltages for parallel circuit.

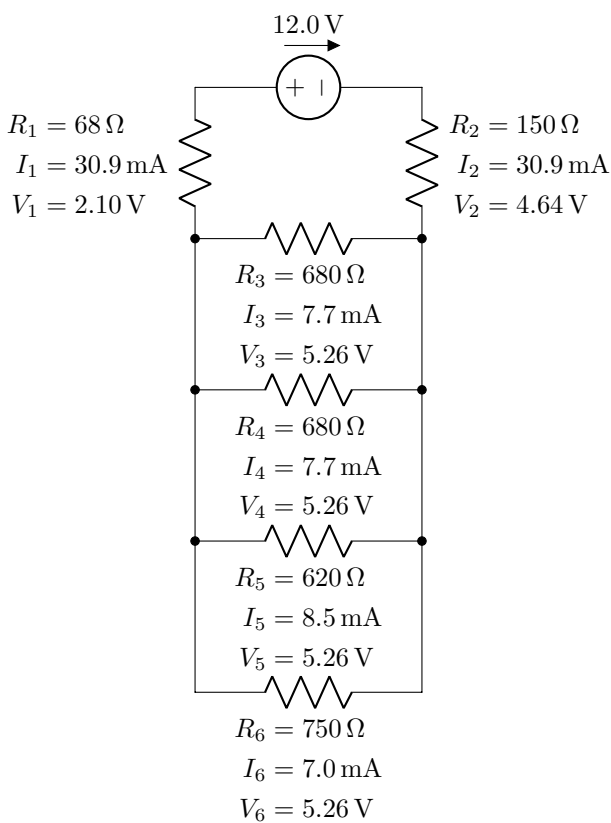


Figure 5: Predicted currents and voltages for complex circuit.

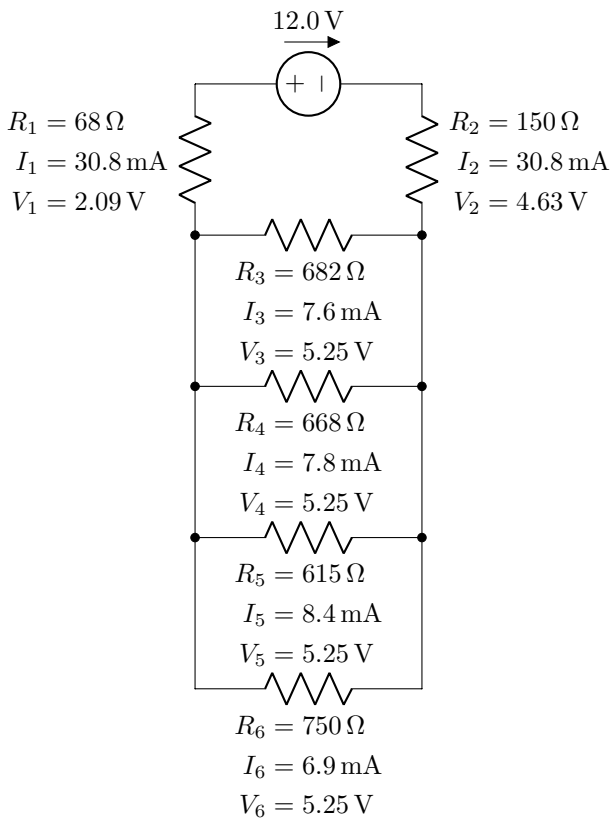


Figure 6: Experimental resistances, currents, and voltages for complex circuit.