



Figure 4: Experimental resistances, currents, and voltages for parallel circuit.