



Figure 2: Experimental resistances, currents, and voltages for series circuit.